

EE 361 ELECTROMECHANICAL ENERGY CONVERSION I

HOMEWORK 2 (DUE: 20/12/2022, 23:59)

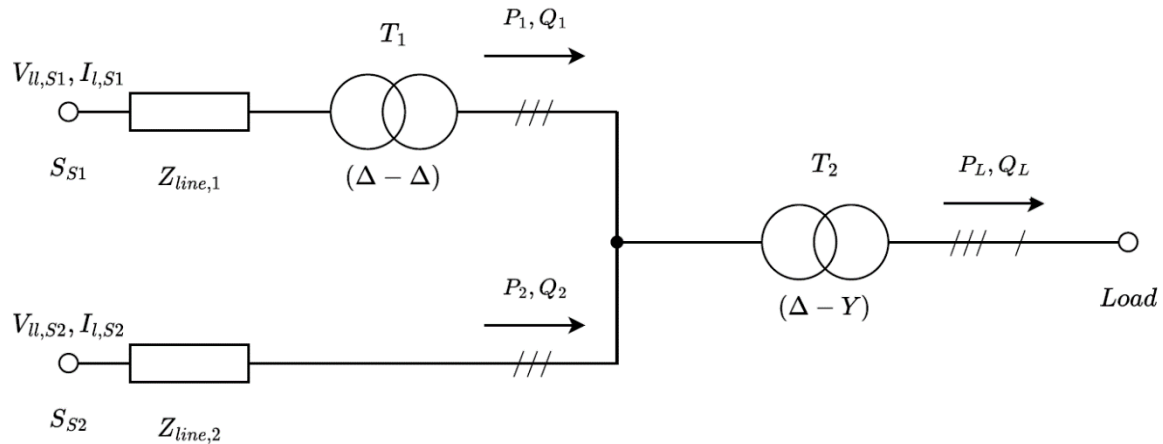


Figure 1 Single-line diagram of a part of a power system

The given single-line diagram shows a part of a power system with two source connections and one load connection.

<p>Transformer 1 (T_1) is built with a single-piece core and has the following characteristics and parameters:</p> <ul style="list-style-type: none"> - $\Delta - \Delta$ connected - 1 MVA - 15kV: 6.9kV - $Z_{T1-HV} = j15.0 \Omega$ - $Z_{T1-LV} = j3.5 \Omega$ 	<p>Transformer 2 (T_2) is composed of three identical single-phase transformers with the following characteristics and parameters:</p> <ul style="list-style-type: none"> - 0.5 MVA - 6.9kV: 230V - $Z_{T2-HV} = 3.0 + j3.0 \Omega$ - $Z_{T2-LV} = 0.003 + j0.003 \Omega$ <p>The single phase transformers are $\Delta - Y$ connected</p>
---	---

Line impedances are $Z_{line1} = 5.0 + j5.0 \Omega$ and $Z_{line2} = 1.0 + j1.0 \Omega$. Core losses and core excitation current of both transformers can be neglected.

The operating condition of the system is given below:

- The power values as denoted in the figure, are as follows:

$$P_1 = 0.8 \text{ MW}, Q_1 = 0.6 \text{ MVar inductive}$$

$$P_L = 1.2 \text{ MW}, Q_L = 0.9 \text{ MVar inductive}$$

- The system is regulated in such a way that rated (nominal) voltage is provided to the load.

According to the given structure and operation conditions, answer the following questions.

Hint: You can use MATLAB Live Script for all type of complex calculations. It will be very convenient to define variables for impedances, voltages, currents and powers.

- a) Why $\Delta - Y$ connection is selected for T_2 ?
- b) Draw an equivalent single-phase circuit referred to as the load side (LV side of T_2) and calculate all impedances of the equivalent circuit.

Hint: In the equivalent circuit leave the referred line impedances in parallel.

- c) Calculate load current (complex) at the defined condition.
- d) Calculate the power factor of the load.
- e) Calculate the voltage regulation of T_2 for the given load case.
- f) Calculate the complex power of source 1 (S_{s1}) and source 2 (S_{s2}).

Hint: You can do calculations by adding up the powers. Do not forget to multiply powers calculated from per-phase equivalent circuit by 3.

- g) Calculate the efficiency of the whole system for the operating condition. Do not forget to account for all three phases.
- h) Calculate source 1 voltage and current amplitudes.

Hints:

In three-phase systems, line currents and line-line voltages are meant if otherwise stated.

You need to calculate the actual values from the values found from per-phase equivalent circuit. Use of line-line voltage ratio is highly suggested.

- i) Calculate source 2 voltage and current amplitudes.